

Program: BE –EXTC

Curriculum Scheme: Choice based R-16

Examination:Second Year Semester III

Course Code: and Course Name: EDC I

SAMPLE QUESTION PAPER


Time: 1 hour

Max. Marks: 50


=====

=====

Note to the students:- All the Questions are compulsory and carry equal marks .

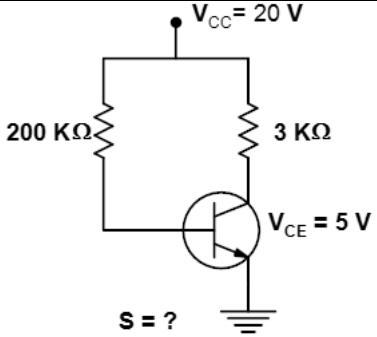Q1.	If for a transistor $\beta = 100$, $I_{CBO} = 10\mu A$, $I_B = 50\mu A$ then $I_E =$
Option A:	10 mA
Option B:	6.06 mA
Option C:	6.06A
Option D:	10A
Q2.	For a transistor $\alpha=0.99$, $I_{CBO}=5\mu A$ and $I_E=8.5$ mA then $I_B =$
Option A:	80 μA
Option B:	75 μA
Option C:	100 μA
Option D:	50 μA
Q3.	
Option A:	100.813
Option B:	80.813
Option C:	52.813
Option D:	50.813

Q4.

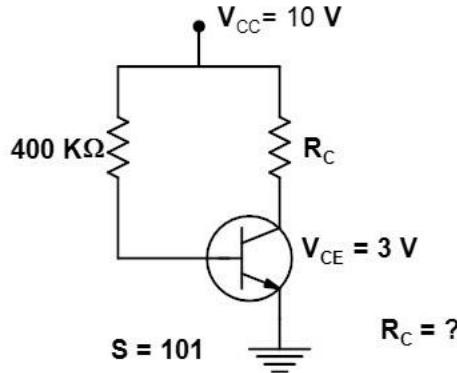


Option A: 2 kΩ

Option B: 5 kΩ

Option C: 2.2 kΩ

Option D: 3 kΩ

Q5.

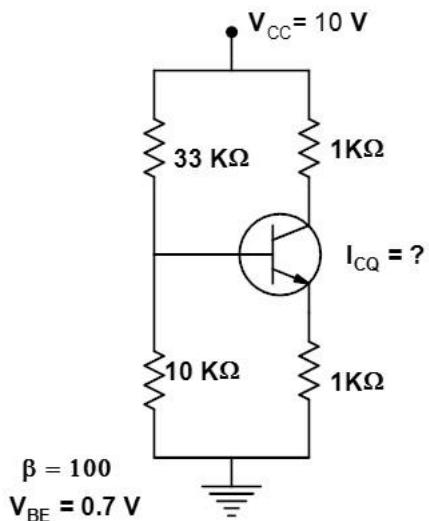

Option A: 1.61 mA

Option B: 2 mA

Option C: 3.13 mA

Option D: 2.61 mA

Q6. For a p-channel FET $V_p = 5 \text{ V}$ $IDSS = 10 \text{ mA}$ and $VGS = 1 \text{ V}$


Option A: 1 mA

Option B: 6.4 mA

Option C: 5 mA

Option D: 1.5 mA

Q7.

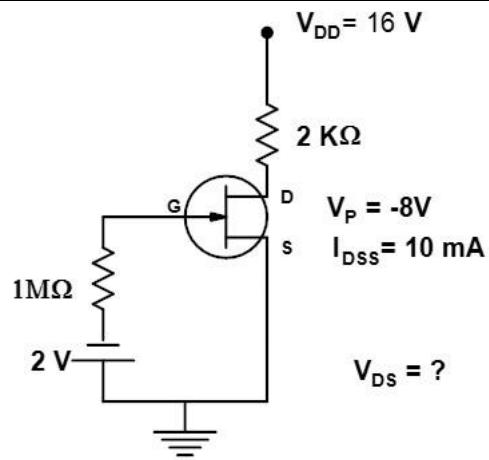


Option A: 8V

Option B: 4.75V

Option C: 5V

Option D: 6V

Q8.

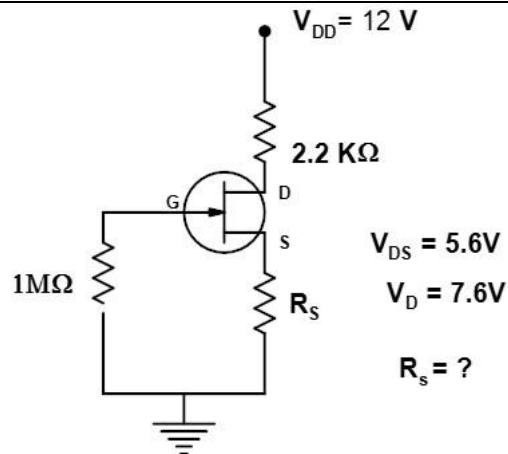


Option A: 1KΩ

Option B: 2Ω

Option C: 5KΩ

Option D: 3KΩ

Q9.

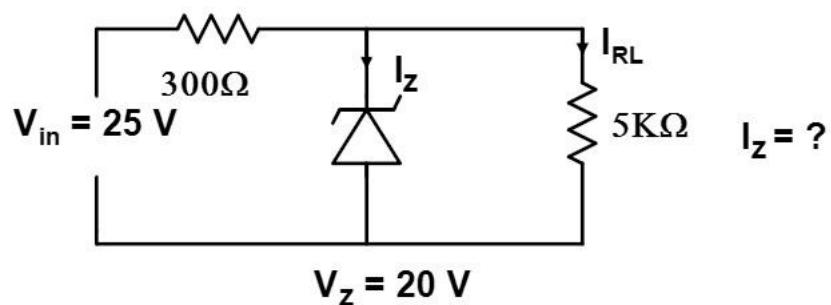

Option A: 10 mA

Option B: 12.67 mA

Option C: 10.57 mA

Option D: 4mA

Q10.	During fabrication process of passive elements to permit selective etching ,the SiO ₂ layer must be subjected to a
Option A:	Oxidation process
Option B:	Epitaxial Growth process
Option C:	Metalization Process
Option D:	Photolithographic Process
Q11.	Average DC voltage of a full wave rectifier circuit is given as
Option A:	$2V_M/\pi$
Option B:	V_M/π
Option C:	$V_M/2\pi$
Option D:	$V_M/2$
Q12.	Consider the simplified diagram of a Zener shunt regulator .The dynamic impedance of zener is 10Ω .Find the voltage stability factor.
Option A:	0.091
Option B:	10
Option C:	11
Option D:	1
Q13.	For an n-channel JFET $V_p= -2V$ the value of V_{GS} for zero current drift will be
Option A:	-2.63V
Option B:	-1.37V
Option C:	+1.37V
Option D:	+2.63V
Q14.	In hybrid pi model of transistor, value of gm and r_π is given by
Option A:	IC_Q/VT and $\beta VT/IC_Q$ respectively
Option B:	$\beta VT/IC_Q$ and IC_Q/VT
Option C:	IC_Q , and βVT
Option D:	None of above
Q15.	While drawing AC equivalent circuit of any amplifier
Option A:	VCC retained and capacitors replaced by short circuit
Option B:	VCC connected to gnd, capacitors replaced by short circuit
Option C:	Capacitors are retained and Vcc connected to gnd
Option D:	None of the above

Q16.	In any two port network if feedback impedance is Z After using Millers theorem Z1 and Z2 are as follows
Option A:	$Z_1 = Z/1-k$, and $Z_2 = Zk/K-1$
Option B:	$Z_1 = Z/K-1$, and $Z_2 = Z/K-1$
Option C:	$Z_1 = ZK/K-1$ and $Z_2 = Z/k-1$
Option D:	None of the above
Q17.	Bipolar junction transistor operates in
Option A:	Can not work as an amplifier and as a switch
Option B:	Saturation as amplifier and active region and cutoff region as a switch
Option C:	Active region as amplifier and canot be used as a switch
Option D:	Active region for amplifier and in cut off and saturation as a switch
Q18.	h parameters of bjt can be found from input, output characteristics
Option A:	hie and hre from input characteristics and hfe and hoe from output characteristics
Option B:	hfe ,hoe from input characteristics and hie and hre from input characteristics
Option C:	hfe ,hre from input characteristics and hie and hoe from input characteristics
Option D:	hre ,hoe from input characteristics and hie and hfe from input characteristics
Q19.	Current flowing into the gate terminal when it is biased in saturation region is
Option A:	Highest
Option B:	Zero
Option C:	lowest
Option D:	None of the above
Q20.	Voltage gain formula for common drain amplifier or souse follower is
Option A:	$gmRs/1+gmRs$
Option B:	$gmRs$
Option C:	1
Option D:	None of the above
Q21.	Factors affecting the bandwidth of RC coupled amplifier
Option A:	Coupling and bypass capacitors and interelectrode capacitors
Option B:	Capacitors do not decide the bandwidth
Option C:	Low frequency and high frequency cut off depends on resistor values
Option D:	None of the above
Q22.	Function of bypass capacitor in CE amplifier is
Option A:	To provide high reactance path for amplified signal appearing at emitter.
Option B:	To provide low reactance path to amplified signal at emitter

Option C:	Output obtained at collector does not change with or without CE
Option D:	CE does not play any vital role in CE amplifier
Q23.	Shockley Equation for JFET is
Option A:	$ID=IDSS[1-VGS/VP]^2$
Option B:	$ID=Vp[1-VGS/Vp]$
Option C:	$Vp=ID[1-VGS/VP]$
Option D:	None of the above
Q24.	Equation for Zero temperature drift for JFET is
Option A:	$ VP-VGS =0.63$
Option B:	$ VGS-VP =0.64$
Option C:	$ VP-VGS =1$
Option D:	None of the above
Q25.	Calculation of value of resistance RD if voltage gain of common source amplifier is given as $ Av =10$, $gm=1.26mS$, $rd=50k$
Option A:	6k
Option B:	5k
Option C:	9.424k
Option D:	3k