

Program: SE Electronics and Telecommunication

Engineering Curriculum Scheme: Revised 2016

(Choice Based) Examination: Second Year Semester

IV

Course Code: **ECC403** and Course Name: **Linear integrated circuits (LIC)**

Time: **1 hour**

Max.

Marks: **50**

=====

Note to the students:- All Questions are compulsory and carry equal marks .

Q1.	In a monostable multivibrator using 555 timer if $R = 100K$ OHMS and $T_{ON}=100ms$ the value of capacitor C is
Option A:	$C = 0.9$ microfarads
Option B:	$C = 1.1$ microfarads
Option C:	$C = 1.9$ microfarads
Option D:	$C = 2.9$ microfarads
Q2.	In Astable multivibrator duty cycle is given by
Option A:	$R_A + R_B / R_A + 2R_B$
Option B:	$R_A / R_A + 2R_B$
Option C:	$R_A + R_B / 2 R_A + R_B$
Option D:	$R_A + 2R_B / R_A + R_B$
Q3.	In 555 timer external AC voltage is applied to which pin to obtain pulse width modulation
Option A:	Discharge pin
Option B:	Reset pin
Option C:	Control Pin
Option D:	Threshold Pin
Q4.	In phased locked loop, PLL
Option A:	Lock in range $F_L >$ capture range F_C
Option B:	Lock in range $F_L <$ capture range F_C
Option C:	Lock in range $F_L =$ capture range F_C
Option D:	Lock in range $F_L > 2 *$ capture range F_C
Q5.	In wide band pass filter quality factor Q is
Option A:	$Q < 10$

Option B:	$Q > 10$
Option C:	$Q = 10$
Option D:	$Q < 1$
Q6.	In voltage controlled oscillator VCO , find free running frequency F_0 . Given R=10K OHMS and C=0.001 microfarads
Option A:	$F_0 = 25 \text{ KHZ}$
Option B:	$F_0 = 35 \text{ KHZ}$
Option C:	$F_0 = 37 \text{ KHZ}$
Option D:	$F_0 = 37.5 \text{ KHZ}$
Q7.	A filter used for rejecton of single frequency HUM of frequency 50 HZ is
Option A:	All pass filter
Option B:	Notch filter
Option C:	Low pass filter
Option D:	High pass filter
Q8.	In band pass filter $F_H=100 \text{ KHZ}$ and $F_L=1 \text{ KHZ}$ then the center frequency F_C is
Option A:	$F_C=10 \text{ KHZ}$
Option B:	$F_C=99 \text{ KHZ}$
Option C:	$F_C=101 \text{ KHZ}$
Option D:	$F_C=150 \text{ KHZ}$
Q9.	In OPamp maximum rate of change of output voltage per unit time is known as
Option A:	Slew rate

Option B:	Input bias voltage
Option C:	CMRR
Option D:	offset voltage
Q10.	Which of the following is the important characteristics of an ideal OPamp
Option A:	$A_V = \infty$, $R_L = \infty$, $R_o = 0$
Option B:	$A_V = \infty$, $R_L = 0$, $R_o = \infty$
Option C:	$A_V = 1$, $R_L = \infty$, $R_o = 0$
Option D:	$A_V = \infty$, $R_L = \infty$, $R_o = 1$
Q11.	The ratio of open loop gain A_V to common mode gain A_{CM} is called
Option A:	Slew Rate
Option B:	Input Biased voltage
Option C:	Differential voltage gain
Option D:	CMRR
Q12.	In an inverting summing amplifier with 2 inputs find the output if $V_1 = 1.5$ V, $V_2 = 3.5$ V and resistors $R_1 = R_2 = R_f = 5.2$ Kohms
Option A:	$V_o = -5$ V
Option B:	$V_o = 5$ V
Option C:	$V_o = -3$ V
Option D:	$V_o = -5.2$ V
Q13.	If we apply square wave at the input of an integrator its output is
Option A:	Cosine wave
Option B:	Triangular wave
Option C:	Spikes at the edges of the square wave
Option D:	Positive going ramp
Q14.	Which element is used in the feedback path of an ideal differentiator circuit
Option A:	Capacitor
Option B:	Resistor
Option C:	Inductor

Option D:	series combination of capacitor and inductor
Q15.	For inverting schmitt Trigger if $R_1=47$ Kohms , $R_2=150$ ohms and $V_{sat}= \pm 12V$.Find threshold voltages and hysteresis voltage V_H .
Option A:	$V_{UT} = 38.17mV$ $V_{LT} = -38.17mV$ $V_H = 76.34 mV$
Option B:	$V_{UT} = 30.17mV$ $V_{LT} = -30.17mV$ $V_H = 60.34 mV$
Option C:	$V_{UT} = 28.17mV$ $V_{LT} = -28.17mV$ $V_H = 56.34 mV$
Option D:	$V_{UT} = 48.17mV$ $V_{LT} = -48.17mV$ $V_H = 96.34 mV$
Q16.	An amplifier circuit using diode in the feedback path of an operational amplifier is called
Option A:	Antilog amplifier
Option B:	Log amplifier
Option C:	Instrumentation amplifier
Option D:	Differential amplifier
Q17.	The time period of output waveform of a square wave generator is given by
Option A:	$T= 2RC \log_e(2R_1 + R_2 / R_2)$
Option B:	$T= RC \log_e(2R_1 + R_2 / R_2)$
Option C:	$T= 2RC \log_e(R_1 + R_2 / R_2)$
Option D:	$T= 2RC \log_e(R_1 + R_2 / 2R_2)$
Q18.	For 5 bit R-2R ladder Digital to Analog converter, find full scale output voltage , if $V_{ref}= 10$ volts.
Option A:	$V_0=1.28 V$
Option B:	$V_0=0.3125 V$

Option C:	$V_0=0.2225V$
Option D:	$V_0=1.68 V$
Q19.	Output voltage of Three terminal IC regulator 7806 is
Option A:	7 V
Option B:	8 V
Option C:	6 V
Option D:	-6 V
Q20.	In IC 723 used as high voltage regulator ,the output voltage is
Option A:	$V_0 > 5V$
Option B:	$V_0 > 7V$
Option C:	$V_0 > 8V$
Option D:	$V_0 > 25V$
Q21.	An IC 723 has $V_0 = 5V$, $I_0=50 \text{ mA}$, $I_{sc} = -75 \text{ mA}$, $V_{sense}=0.6 \text{ V}$ at temperature of 26 degree celsius. Then value of resistor R_{sc} is
Option A:	$R_{sc} = 8 \text{ ohms}$
Option B:	$R_{sc} = 7.8 \text{ ohms}$
Option C:	$R_{sc} = 6 \text{ ohms}$
Option D:	$R_{sc} = 6.8 \text{ ohms}$
Q22.	A popular Three terminal voltage regulator IC which provides adjustable positive volatage is
Option A:	79 XX
Option B:	78 XX
Option C:	LM317
Option D:	LM399
Q23.	In 3 terminal fixed voltage regulator difference between the unregulated input volatage V_{in} and output voltage V_0 is called
Option A:	Input bias voltage
Option B:	Differential voltage
Option C:	Drop out voltage
Option D:	Drop in voltage
Q24.	In Active RC phase shift oscillator,frequency of oscillation is 5KHZ.IF capacitor value is 0.01microfarads,then value of resistor R is
Option A:	$R=2.33\text{kohms}$
Option B:	$R=1.29\text{kohms}$

Option C:	R=2.83kohms
Option D:	R=4.33kohms
Q25.	The difference between the currents flowing into the inverting and noninverting terminals of Opamp is called
Option A:	Bias current
Option B:	input offset Current
Option C:	drift current
option D:	thermal drift